

EE 618 2018 [ZELE]


Course Projects I and II


Project I

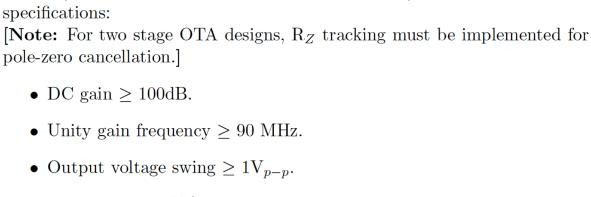Design an Operational Transconductance Amplifier in SCL 180nm technology (fully differential input, single ended output) to meet the following



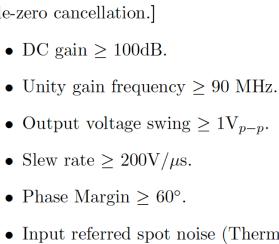

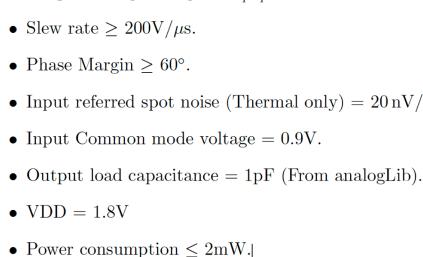

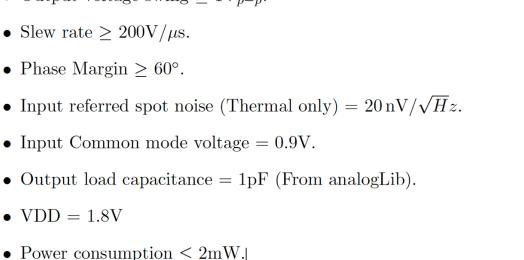

Specifications

Course Project - I

- Design and Simulate the OTA to meet the specifications (SCL 180nm technology)
- Hand calculations must.
- Supporting documents are provided on moodle Simulations / Analysis details Test Benches
- Report template (Must be typed)
 Please follow the template unless you can do something better
 Show all relevant calculations

Course Project I – Grading (10% overall)

Reports will be graded (50 points) based on the following grading criteria:


Initial design/Hand calculations	10
Simulation results	20
Quality of report	10
Viva	10
Bonus (Architectures)	+ 12.5

- BONUS Architectures: Folded cascode, Gain boosting, Slew rate enhancement, Rail-to-rail OTA or any other architecture.
- Viva will focus on the explanation of design flow and showing results on your laptop.

Course Project - II

- Students will layout the OTA designed in Course Project I
- Layouts common centroid and other matching techniques
- Schematic and Post layout simulations
- Poster presentation Invited Guests

Example OTA Layout

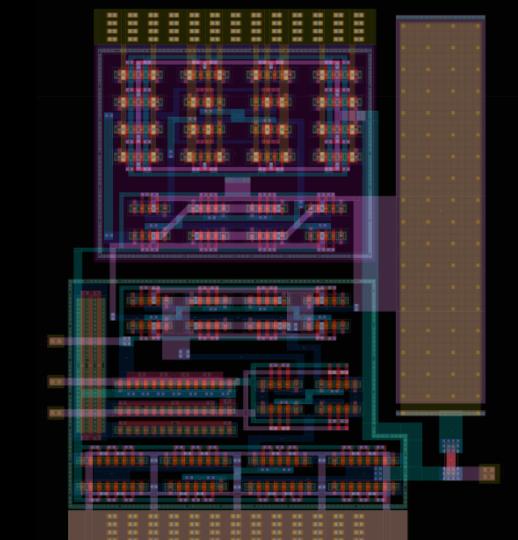

TIMELINE

- Project I uploaded
- Project II uploaded

- Hand-calculations reviewed by TAs
- Project I Final Report submission
- Project I Viva
- Project II Final Report submission
- Project II Viva/Poster Presentation

25th September 10th October

3rd October

15th October

17th October

5th November

10th November